

# Lab Work

## CPT-based Cs microcell atomic clock

2022

### Contents

<b>1</b>	<b>Basics on miniature atomic clocks</b>	<b>1</b>
<b>2</b>	<b>Presentation of the CPT clock experiment</b>	<b>2</b>
<b>3</b>	<b>Lab work</b>	<b>4</b>
3.1	Initial configuration . . . . .	4
3.2	VCSEL diode laser response . . . . .	5
3.3	Linear spectroscopy . . . . .	5
3.4	Towards CPT spectroscopy . . . . .	6
3.5	Close the atomic clock loop . . . . .	9

## 1 Basics on miniature atomic clocks

Figure 1 shows the architecture of a miniature Cs cell atomic clock based on coherent population trapping (CPT).

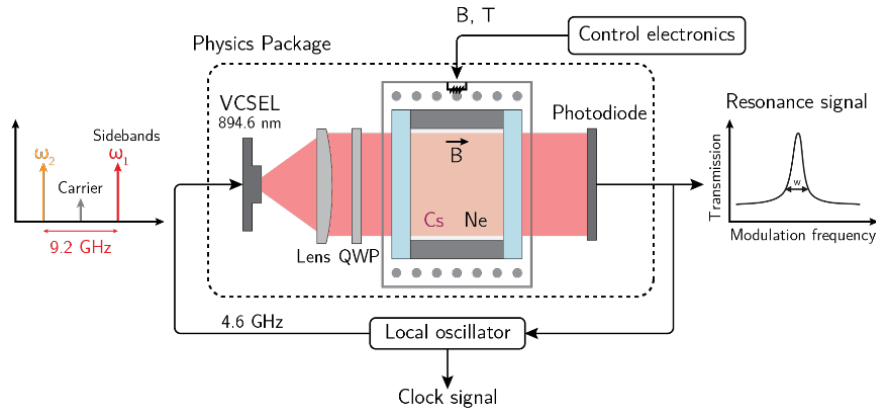


Figure 1: Simplified architecture of a buffer-gas filled Cs microcell CPT atomic clock.

Cs vapor is filled in a glass-silicon-glass micro-fabricated cell whose technology is described in [1]. The Cs cell is filled with a pressure buffer gas. The buffer gas slows down atoms in the microcell and increases the time for the atoms to reach the cell walls. It also reduces the first-order Doppler effect and leads to operation in the Lamb-Dicke regime [2]. Eventually, it helps to detect narrow CPT resonances.

Atoms in the cell interact with a dual-frequency (in the ideal case!) optical field generated by a VCSEL laser whose injection current is directly modulated at 4.596 GHz through a bias-tee. This generates two first-order optical sidebands separated by about 9.192 GHz, required to produce the CPT interaction. The laser output beam crosses a neutral density filter to attenuate the optical power and a quarter-wave plate to polarize circularly the optical beam. The light transmitted through the cell is detected by a photodiode.

When the frequency difference between both first-order optical sidebands exactly equals the Cs ground-state hyperfine splitting (9.192 631 770 GHz), atoms are trapped through a quantum interference process in a quantum superposition of both ground states (see Fig. 2). In this so-called dark state, the light atomic absorption is reduced and the atomic vapor transparency is increased. The CPT resonance linewidth is ultimately limited by the microwave CPT coherence relaxation time and can be measured to be of about 1 kHz in a buffer-gas filled micro-fabricated cell. The signal at the output of the photodiode is used in two main servo loops. The first one is dedicated to the stabilization of the laser frequency onto the bottom of a homogeneously broadened optical line. The second loop stabilizes the local oscillator (LO) frequency onto the atomic clock transition.

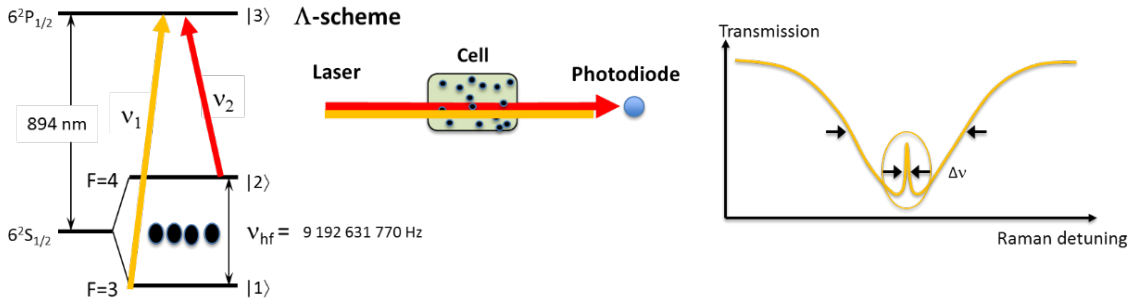


Figure 2: Basic principle of CPT.

## 2 Presentation of the CPT clock experiment

Figure 3 shows the table-top experiment environment. The oscilloscope was used to monitor the output of the photodiode, but it is not needed any more since the monitoring is now done in the software.

Figure 4 shows a zoom on the clock-card that is now inside the clock case.

### Important points:

VCSEL : 894.6 nm (Cs D1 line); Microcell: Cs-Ne ( $\approx 76$  Torr), heated at about 75°C. The cell length is 1.4 mm. Its diameter is 2 mm. The static magnetic field applied along the cell can be tuned using a current value. It is applied in order to lift the Zeeman degeneracy.

Figure 5 shows the typical interface program window to pilot the clock. A C program was implemented to pilot a microcontroller through an Arduino platform. An upgraded python interface has been developed this year. We have done our best to make it as stable as possible but it is the first time it is tested live, so please report any bug.

The program is launched from a Jupyter Notebook which should be already running on your labwork computer.

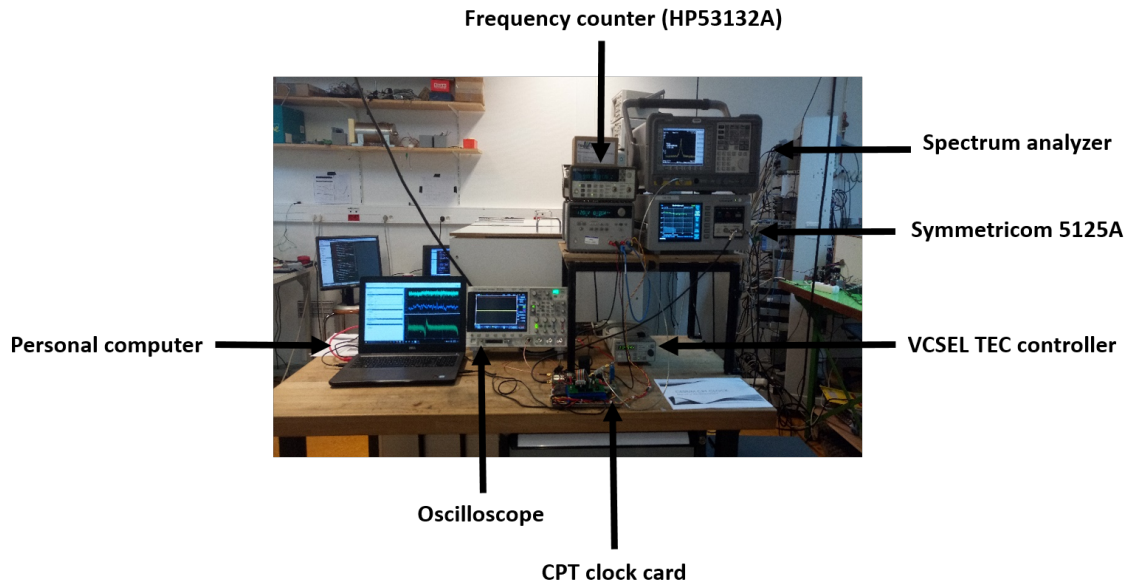


Figure 3: Table-top CPT experiment environment. From left to right: personal computer to pilot the experiment, oscilloscope to monitor signals, the CPT clock card including physics package and all embedded electronics, a Thorlabs TEC200C controller used to stabilize the VCSEL temperature. On the top-right, a power-supply to drive the clock-card, a frequency counter (HP53132A), a spectrum analyzer used to monitor the local oscillator microwave signal at 4.6 GHz and a Symmetricom 5125A test-set to measure the clock Allan deviation. A hydrogen maser 10 MHz signal cable is also available.

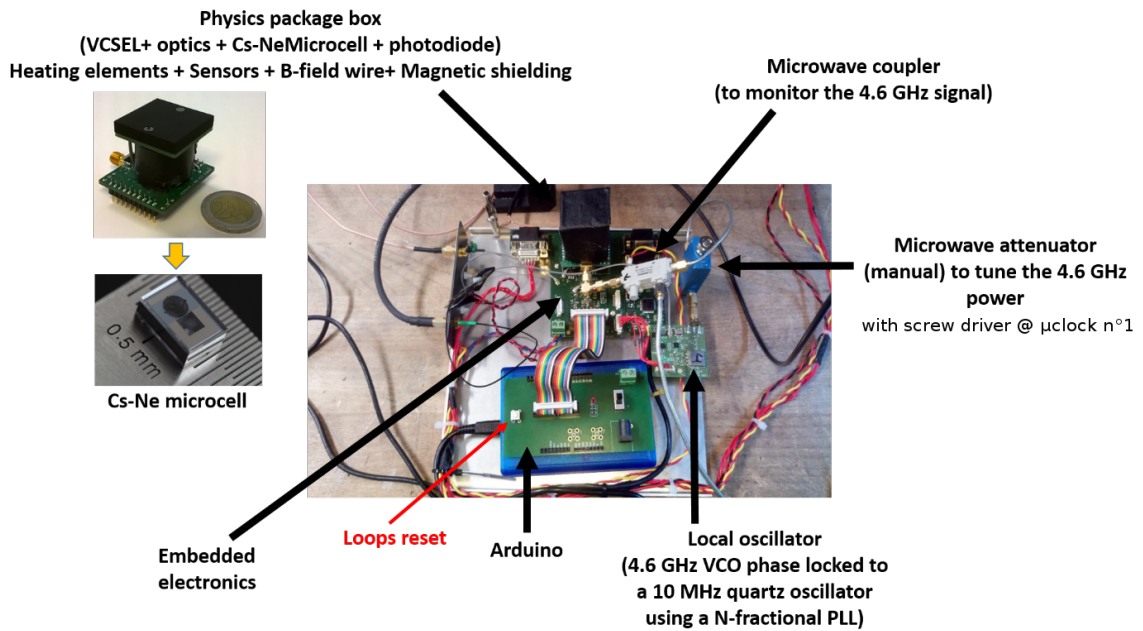


Figure 4: Details of the clock-card.

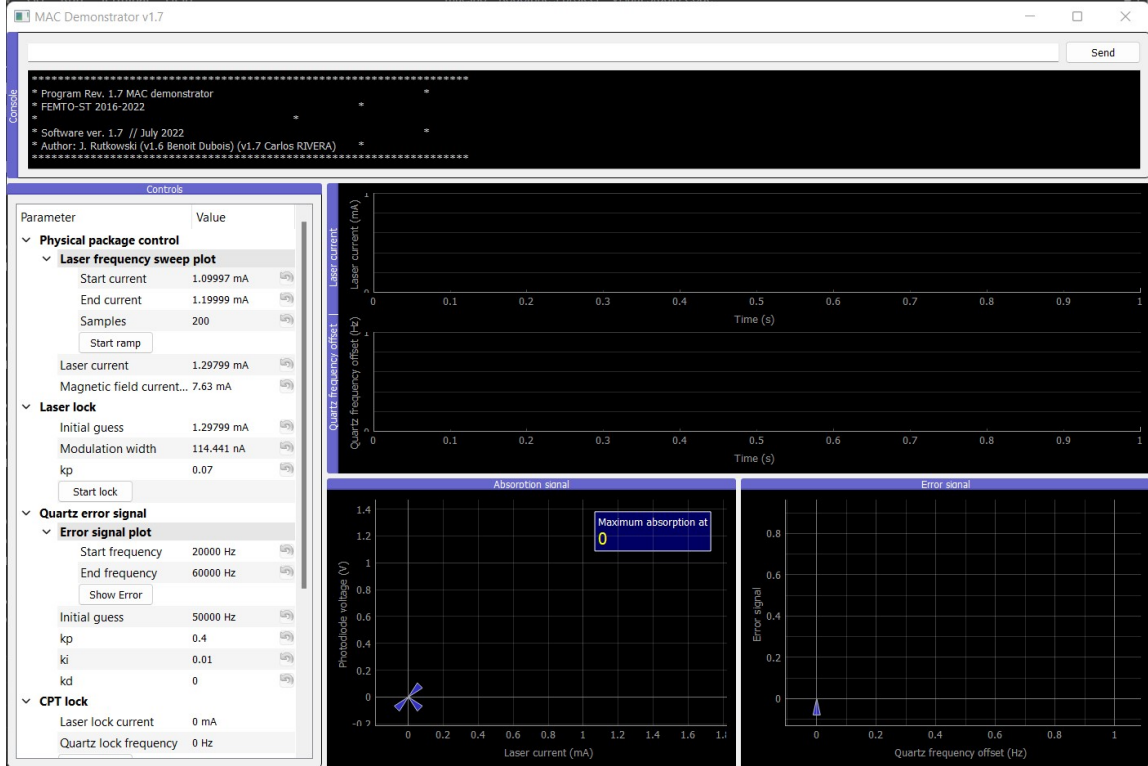


Figure 5: Program graphic interface.

### 3 Lab work

#### 3.1 Initial configuration

The laser temperature set-point has been pre-set using the Thorlabs TED200C. It is set at 75°C (1.609 kΩ) for the clock 1, around 80°C (1.206 kΩ) for the clock 2 and around 70°C (1.866 kΩ) for the clock 3 . For the first step, the 4.6 GHz signal power is turned off by the microwave attenuator at the output of the local oscillator card (the sliders 1 to 6 are set to “1”, see Fig. 6). The microwave attenuator is accessible on the side on the clock case.

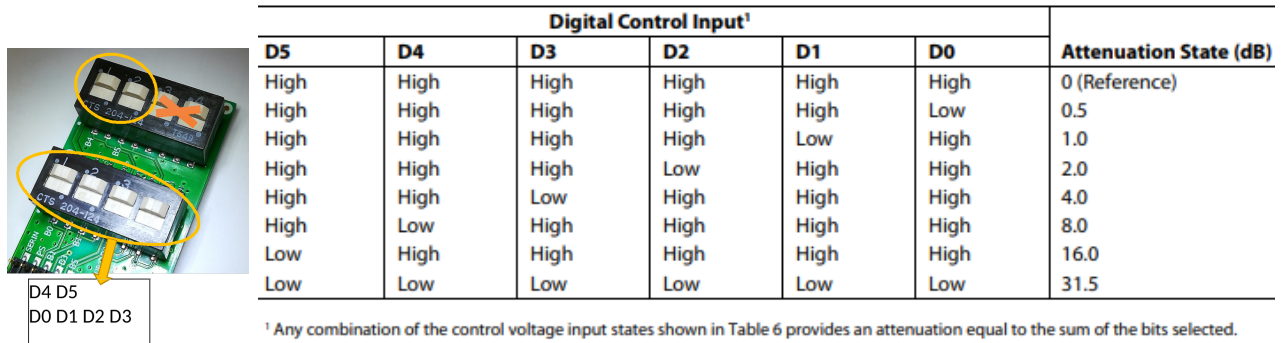


Figure 6: (Left) Localization of the sliders for the 0.1 GHz to 6.0 GHz, 0.5 dB LSB, 6-bit, silicon digital attenuator. MSB = Most Significant Bit, LSB = Least Significant Bit. (Right) Attenuation table for the 0.1 GHz to 6.0 GHz, 0.5 dB LSB, 6-bit, silicon digital attenuator.

### 3.2 VCSEL diode laser response

**Manipulation 1.** The goal is to measure the *lasing threshold* of the VCSEL, *ie* the current above which the output power becomes roughly linear with the laser current. For this purpose, ramp the laser current from 0 to 1.7 mA. To do this, enter the start and end currents of the sweep in the control box and then press the **Start ramp** button, as shown in figure 7. Observe the output of the photodiode on an oscilloscope (NOT with the built-in **Absorption signal** graph as you would undergo saturation of ADCs connected to the Arduino). Identify the threshold current value and set the diode current at this value.

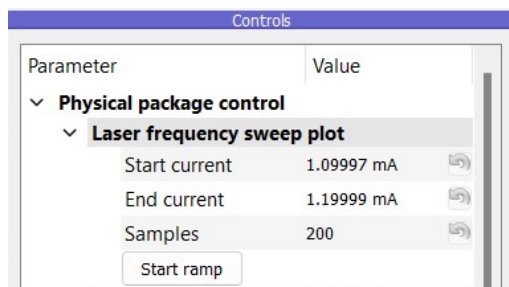


Figure 7: Screenshot of the control panel for laser current ramps. Enter your chosen values (stay below 1.8 mA!) and press **Start ramp** to update the display at the bottom-left of the screen (photodiode voltage vs laser current).

### 3.3 Linear spectroscopy

**Manipulation 2.** Tune the laser current above the lasing threshold using the laser control box interface. The goal is now to sweep the laser frequency; this is done by sweeping the laser current. To do this, enter the start and end currents of the sweep in the control box and then press the **Start ramp** button, as shown in figure 7. Typical scan amplitudes should be 0.1 mA. Disconnect the oscilloscope until the end of the lab (this will reduce the noise of the signal), and observe the signals in the **Absorption signal** graph at the bottom-left of the screen. It is possible to determine the number of samples to be displayed in the **Absorption signal** graph for a higher resolution.

Look at the spectrum obtained on the **Absorption signal** graph and/or the oscilloscope. If required, tune the start and end current, as well as the laser temperature. Explain what you observe.

**Question 1.** Identify and name the different optical transitions of the Cs  $D_1$  line. For reminder, the figure 8 reports the Cs  $D_1$  line energy structure. Identify the transitions 3-3', 3-4', 4-3' and 4-4'.

**Question 2.** Calibrate the x-axis to determine roughly the laser frequency variation for a given change in laser current.

**Question 3.** Measure the linewidths of the optical transitions. Given the cell temperature  $T \approx 80^\circ\text{C}$  and the Neon buffer gas broadening coefficient  $\beta \approx 11 \text{ MHz/Torr}$ , estimate the buffer gas pressure  $p$ .

**Question 4.** Estimate the optical absorption of the cell (the percentage of laser power absorbed by the cell). The Beer-Lambert law, assuming that we operate in an optically thin medium, could help you to estimate the actual cell temperature. Here, knowing the cell length  $L = 1.4 \text{ mm}$  and the broadened linewidth, you can estimate the Cs atomic density inside the cell and the Cs partial pressure  $p_{Cs}$ .

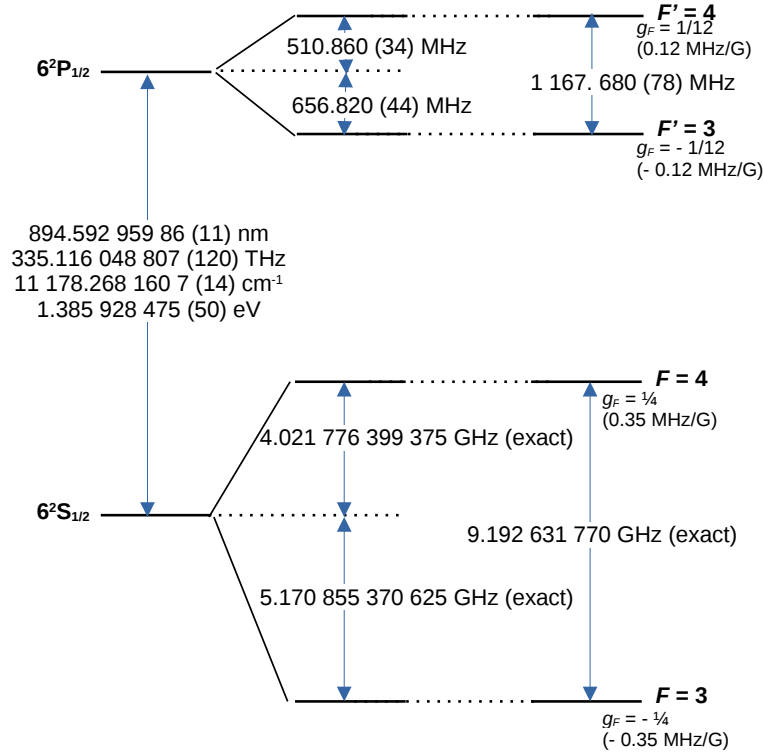


Figure 8: Atomic levels of Cs.

**Note:** one could fit this spectrum by a sum of four Voigt profiles to estimate the absorption lines broadening. This broadening results from the sum of the optical transition natural linewidth, the Doppler broadening and an additional broadening due to the presence of buffer gas. By using the optical density and the line broadening measurements, one can extract both the temperature and buffer gas pressure of a particular cell. Here, you can estimate the expected Doppler broadening and see how different your measured linewidth is.

$$\Delta\nu_D = \frac{2\nu_{\text{opt}}}{c} \sqrt{\frac{2RT}{M} \ln 2}, \quad (1)$$

with  $\nu_{\text{opt}} = 335$  THz,  $R = 8.31$  J/(mol.K),  $M = 133$  g/mol.

### 3.4 Towards CPT spectroscopy

We now start to implement CPT spectroscopy.

**Manipulation 3.** Now turn on the 4.6 GHz microwave signal and increase progressively its power using the microwave attenuator. To do this, you can set the attenuators sliders to 0, starting from the bottom-left slider. Note that you can read the actual microwave power by monitoring the spectrum analyzer. This measured power is 20 dB (20dB-coupler) lower than the one actually experienced by the VCSEL bias tee.

**Question 5.** What do you observe when you scan again the laser frequency? Explain.

Set the microwave power (read on the spectrum analyzer) to - 25 dBm. To detect a CPT signal, we need to ensure that the laser frequency is tuned (ideally “stabilized” in a real miniature atomic clock using a lockin amplifier-based modulation-demodulation technique applied on the laser current) such that the laser is connected to a given excited state. For this purpose, the laser frequency must



be adjusted such that the photodiode output signal is tuned on the bottom of a “CPT-resonant” broadened optical line (the one that appeared between both initial doublets of the Cs D1 line!).

**Question 6.** You first need to determine the diode current at the bottom of the central absorption line. To do so, the plotting tool **Show minimum** from the control panel can be used, which automatically identifies the lowest voltage measured in the running scanning ramp, as show in figure 9, if needed the ramp limits can be tuned.

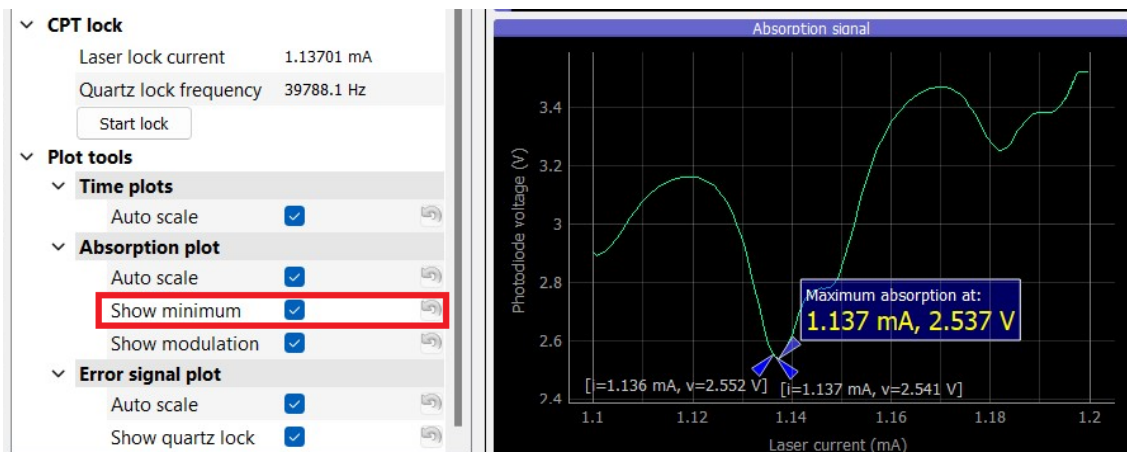


Figure 9: Screenshot of the bottom left of the control program, showing the plotting tools and the absorption curve.

**Manipulation 4.** Switch off the laser ramp by clicking the **Stop ramp** button on the program (figure 10) or using the external reset button on the clock case.

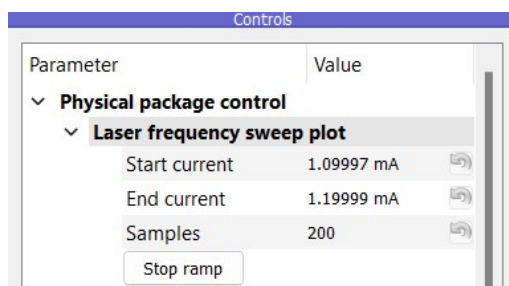


Figure 10: Screenshot of the stop button of the control program.

First, you can set the laser current to the desired value in the **Laser frequency sweep plot** panel. Check that you observe the expected absorption value.

Then, you can engage the laser lock. This is done using the **Laser lock** control panel (see Fig. 11). Provide in the initial **guess** box the value you found previously and start with a modulation width of about 100 nA and  $k_p \approx 0.05$  and start the lock. Make sure the laser current is locked by checking the laser current vs time curve displayed in the program. You can optimize the modulation width and  $k_p$  parameters to improve the lock.

**Question 7.** Comment on what happens on the photodiode signal. Write down the laser current where the laser lock has stabilized.

**Manipulation 5.** Once the laser frequency is well-adjusted, we can try to detect the CPT resonance by scanning the local oscillator frequency. First click **Stop lock** on the program (in the

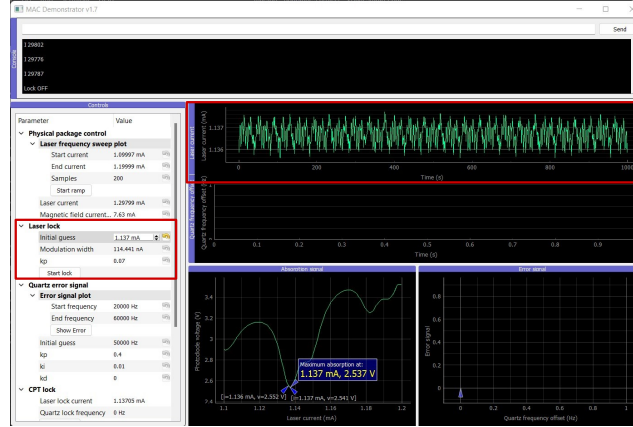


Figure 11: Screenshot of the software with focus on the laser lock control panel and the laser current vs time graph.

"Laser lock" panel) or press the “Reset” button on the clock case. Using the **Quartz error signal** panel from the software (see Fig. 12), tune the scan parameters for the ramp. You can scan the quartz frequency between 0 and 60 kHz. Press the **Show error** button to display the graph. You can check on the spectrum analyzer that this scans the local oscillator frequency around a center frequency of 4.596340xxx GHz.

Here, you should detect the CPT signal (CPT error “demodulated” signal in fact) in the bottom CPT error signal scan window. Note that the signal to noise ratio of the CPT signal can be significantly increased by tuning finely the laser optical frequency in the laser current line of the **Laser frequency sweep plot** panel.



Figure 12: Screenshot of the software with focus on the quartz error signal control panel and graph.

**Question 8.** Estimate the CPT signal linewidth in Hz and the CPT signal amplitude (arb. units).

**Manipulation 6.** Do this measurement for several values of the 4.6 GHz signal power (-29 to -24 dBm) and note for each case the CPT signal amplitude. Note: Each time you change the microwave power, re-adjust the laser current to be on the bottom of the good optical absorption line (laser current line of the **Laser frequency sweep plot** panel), before you start the quartz ramp.

**Question 9.** Plot the CPT signal amplitude (arb. units) versus the microwave power. Explain



the result.

**Manipulation 7.** Now reduce the value of the static magnetic field current. What do you observe? Record the CPT spectrum for a few values of the static magnetic field. This measurement could help you to know the actual static magnetic field experienced by the atoms. Indeed, magnetic-sensitive Zeeman transitions are shifted by about 700 kHz/G (see Fig. 8).

From this, note that the best way to know the actual magnetic field variations experienced by the atoms is to stabilize the local oscillator frequency onto one the magnetic-field sensitive Zeeman transition. In this case, fluctuations of the clock frequency are expected to be mainly due to this effect.

### 3.5 Close the atomic clock loop

**Manipulation 8.** Set the microwave power at -25 dBm. Tune the laser current to the bottom of the good absorption line (laser current line of the **Laser frequency sweep plot** panel).

Give the right initial guess value in the **Quartz error signal**>**Error signal plot** control panel (see Fig. 13).

Engage the lock by pressing the **Start lock** button of the **CPT lock** control panel. The current values for the (locked) laser current and quartz offset frequency can be read in the **CPT lock** control panel.



Figure 13: Screenshot of the software with focus on the quartz error signal control panel, start lock button and error signal graph and stabilization of quartz frequency.

The the **Start lock** button of the **CPT lock** control panel stabilizes both the laser frequency and the local oscillator frequency onto the CPT resonance frequency. For both servo loops, a digital lock-in amplifier technique is applied. In clock closed loop operation, the frequency synthesizer is used to scan successively on both sides of the CPT resonance. An error signal, proportional to the Raman detuning, is generated and processed in a PI controller system to correct the 10 MHz quartz oscillator pilot frequency (quartz voltage tuning). The output useful signal is the signal from the 10 MHz quartz oscillator, locked to the atoms.

**Manipulation 9.** Check that the servo loop is OK (stabilization of the laser current and LO frequency going to the correct frequency). You can adjust  $k_p$ ,  $k_i$  and  $k_d$  parameters of the quartz lock in the the **CPT lock** control panel. Possible initial values are  $k_p = 0.4$ ,  $k_i = 0.01$  and  $k_d = 0$ .

**Manipulation 10.** You can then measure the clock Allan deviation using the Symmetricom test setup (see Fig. 14).

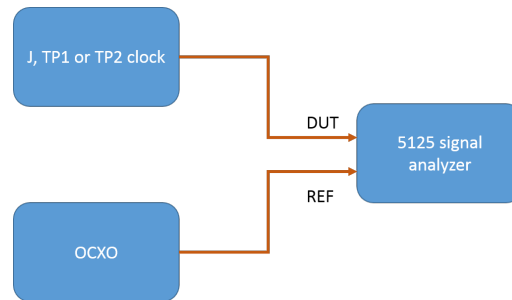


Figure 14: Clock Allan deviation measurement setup.

**Manipulation 11.** To do so, we will compare the labwork clocks with very stable OCXOs (oven-controlled quartz oscillators). Before measuring the clock fractional frequency instability, it is necessary to verify the OCXO performance. To do so, one can input two different OCXO signals to the 5125 signal analyzer.

You can then plug the clock LO signal at 10 MHz to the DUT port, while the OCXO signal at 5 MHz is sent to the REF port. Establish the clock short-term performance, as well as the OCXO frequency drift.

You can then compare short-term stability performances in both free-running and locked regimes.

**Question 10.** How would you estimate the clocks stability if you did not have a good OCXO to compare it to? Propose a first measurement that can help obtaining an estimate using two clocks.

Is there a way to know the actual individual clocks stabilities given that there are four Labwork clocks?

**Manipulation 12.** If there is any time left, you can go ahead and try to use one of the two above solutions.

## References

- [1] M. Hasegawa et al., Sensors Actuators 167, 594-601 (2011)
- [2] R. H. Dicke, Phys. Rev. 89, 472 (1953)