

Lab Work

CPT-based Cs microcell Atomic Clock

Important Note:

This lab-work is a very recent lab work for EFTS 2018. Efforts would need to be pursued on to optimize it. We are aware that the setup, control software, lab-work text and clock performances need to be improved.

You will be the first users of these lab-work prototypes. We apologize in advance for potential issues.

The clock prototypes have been assembled recently and remain fragile prototypes, embedding fragile key components. Manipulate the clock cards with extreme precaution during the lab-work.

If any doubt, contact the lab-work responsible for help.

NOTES POUR 2019 :

Intégrer gnuplot et procédure FIT VOIGT pour faire analyse quantitative (déduire température cellule, pression néon, densité Cs)

Mettre les étudiants à l'intérieur du U si TP en salle de réunion IPV

Mettre en valeur les mesures attendues / les questions posées, soit sous forme 1. 2. 3., soit italique ou gras

VERIFIER ADRESSES SOFT/DONNEES AVEC GIL

A la fin, faire un uncertainty budget ?

+ three-corner ? ou on fait des battements deux à deux. => faire d'abord mesures par groupe contre quartz Rackon ; puis les mettre ensemble pour qu'ils proposent une méthode pour caractériser les horloges sans utiliser les quartz (ie TCH ou Grovariance) à voir selon matos et cours dispos.

1/ Basics on miniature atomic clock

Figure 1 shows the architecture of a miniature Cs cell atomic clock based on coherent population trapping (CPT).

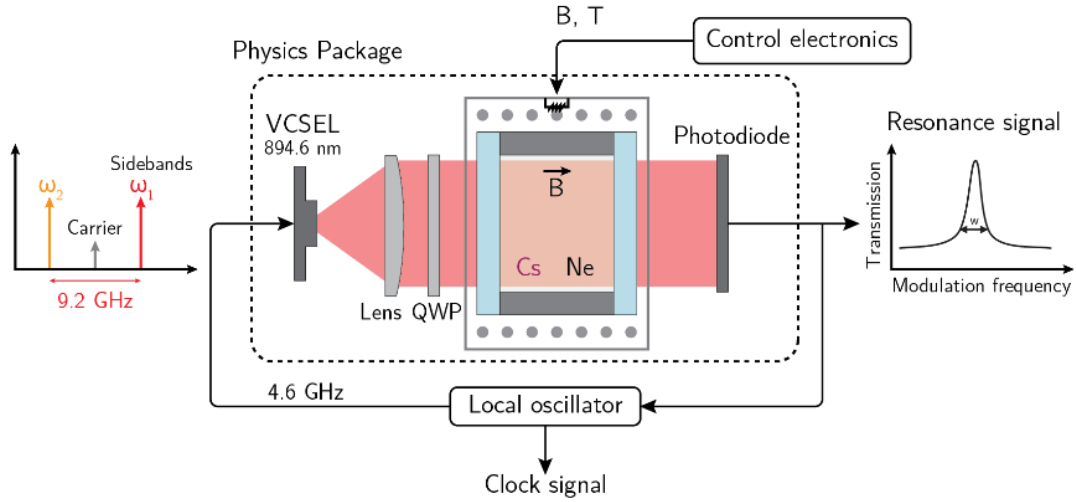


Figure 1: Simplified architecture of a buffer-gas filled Cs microcell CPT atomic clock.

Cs vapor is filled in a glass-silicon-glass micro-fabricated cell whose technology is described in [1]. The Cs cell is filled with a pressure buffer gas. The buffer gas allows to slow down atoms in the microcell and to increase the time for the atoms to reach the cell walls. The presence of buffer gas allows to reject the first-order Doppler effect and to operate in the Dicke regime [2]. The presence of buffer gas helps to detect narrow CPT resonances. The cell is heated at about 75°C. A static magnetic field is applied in order to lift the Zeeman degeneracy.

Atoms in the cell interact with a dual-frequency (in the ideal case!) optical field generated by a VCSEL laser whose injection current is directly modulated at 4.596 GHz through a bias-tee. This allows to generate two first-order optical sidebands separated by about 9.192 GHz, required to produce the CPT interaction. The laser output beam crosses a neutral density filter to attenuate the optical power and a quarter-wave plate to polarize circularly the optical beam. The light transmitted through the cell is detected by a photodiode.

When the frequency difference between both first-order optical sidebands exactly equals the Cs ground-state hyperfine splitting (9.192 631 770 GHz), atoms are trapped through a quantum interference process in a quantum superposition of both ground states (see Fig. 2). In this so-called dark state, the light atomic absorption is reduced and the atomic vapor transparency is increased. The CPT resonance linewidth is ultimately limited by the microwave CPT coherence relaxation time and can be measured to be of about 1 kHz in a buffer-gas filled micro-fabricated cell. The signal at the output of the photodiode is used in two main servo loops. The first one is dedicated to stabilize the laser frequency onto the bottom of a homogeneously broadened optical line. The second loop allows to stabilize the local oscillator (LO) frequency onto the atomic clock transition.

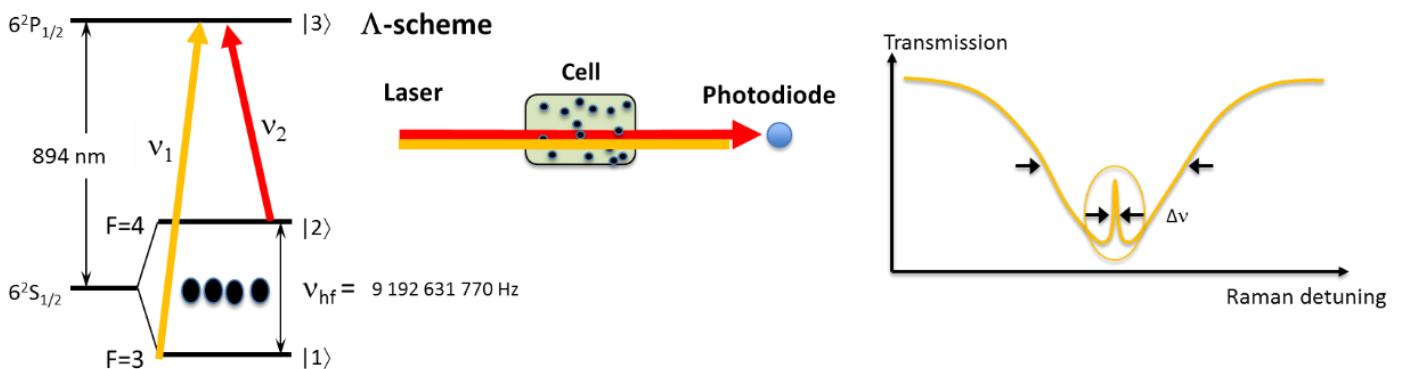


Figure 2: Basic principle of CPT.

2/ Presentation of the CPT clock experiment.

Figure 3 shows the table-top experiment environment.

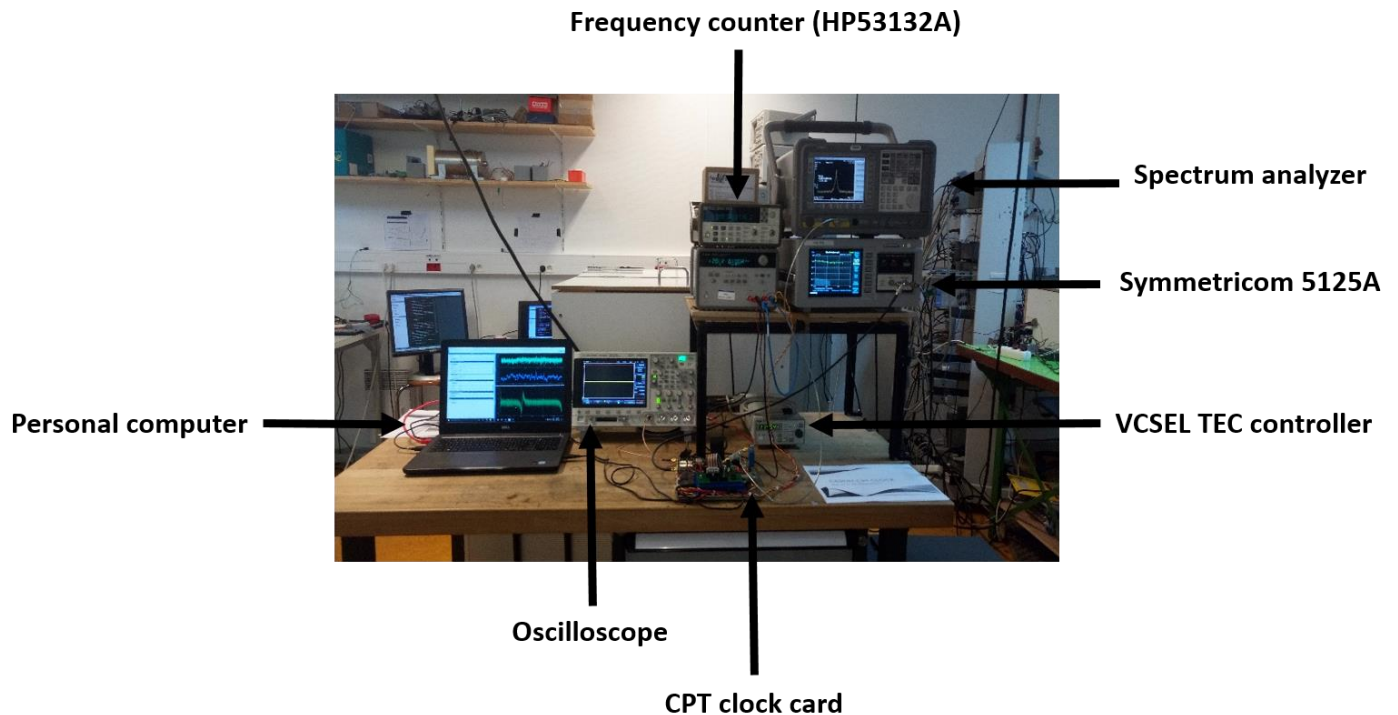


Figure 3: Table-top CPT experiment environment. From left to right: personal computer to pilot the experiment, oscilloscope to monitor signals, the CPT clock card including physics package and all embedded electronics, a Thorlabs TEC200C controller used to stabilize the VCSEL temperature. On the top-right, a power-supply to drive the clock-card, a frequency counter (HP53132A), a spectrum analyzer used to monitor the local oscillator microwave signal at 4.6 GHz and a Symmetricom 5125A test-set to measure the clock Allan deviation. A hydrogen maser 10 MHz signal cable is also available.

Figure 4 shows a zoom on the clock-card.

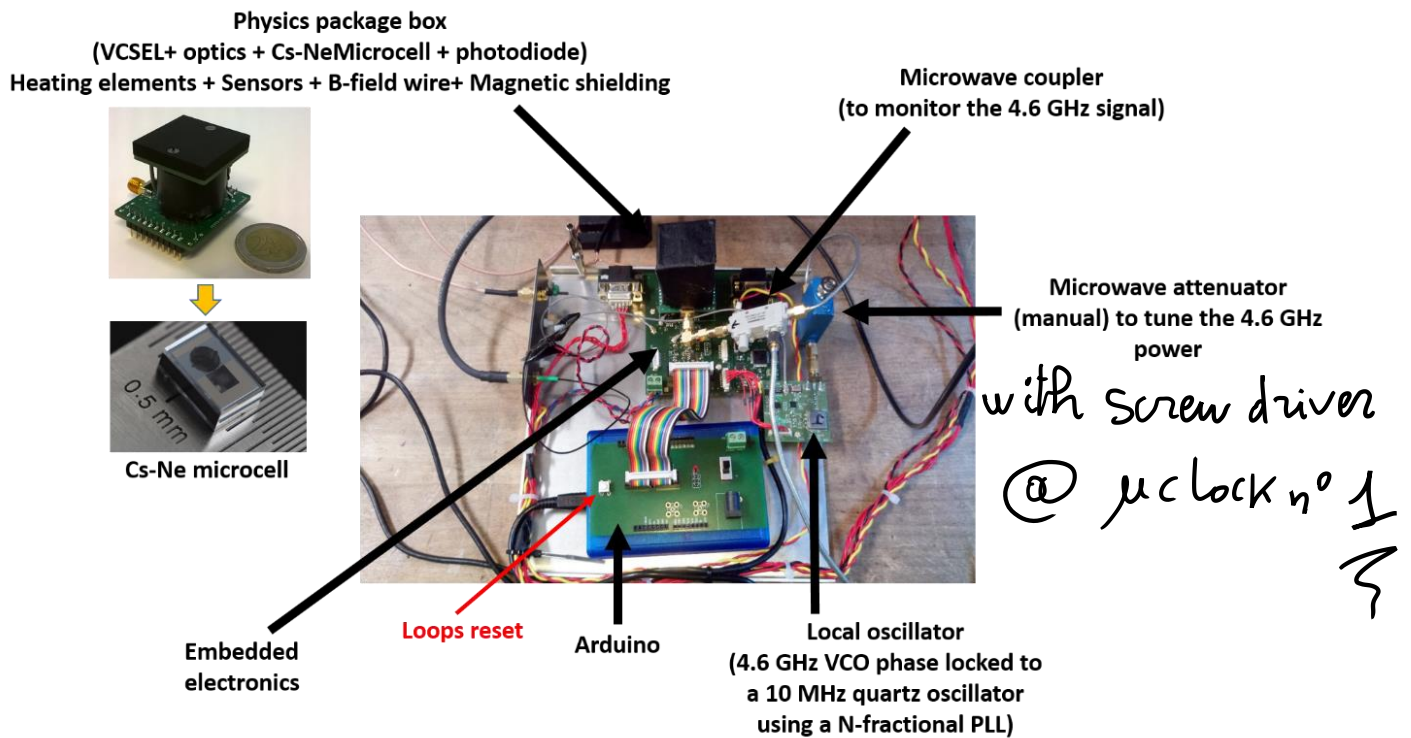


Figure 4: Details on the clock-card

Important points:

VCSEL : 894.6 nm (Cs D₁ line)

Microcell: Cs-Ne (~76 Torr), heated at about 75°C. The cell length is 1.4 mm. Its diameter is 2 mm.
The static magnetic field applied along the cell can be tuned using a current value.

Figure 5 shows the typical interface program window to pilot the clock. A C program was implemented to pilot a microcontroller through an Arduino platform. A preliminary Python interface was developed to operate the clock. You can visualize the commands and digital words sent to the micro-controller at any time in the command window.

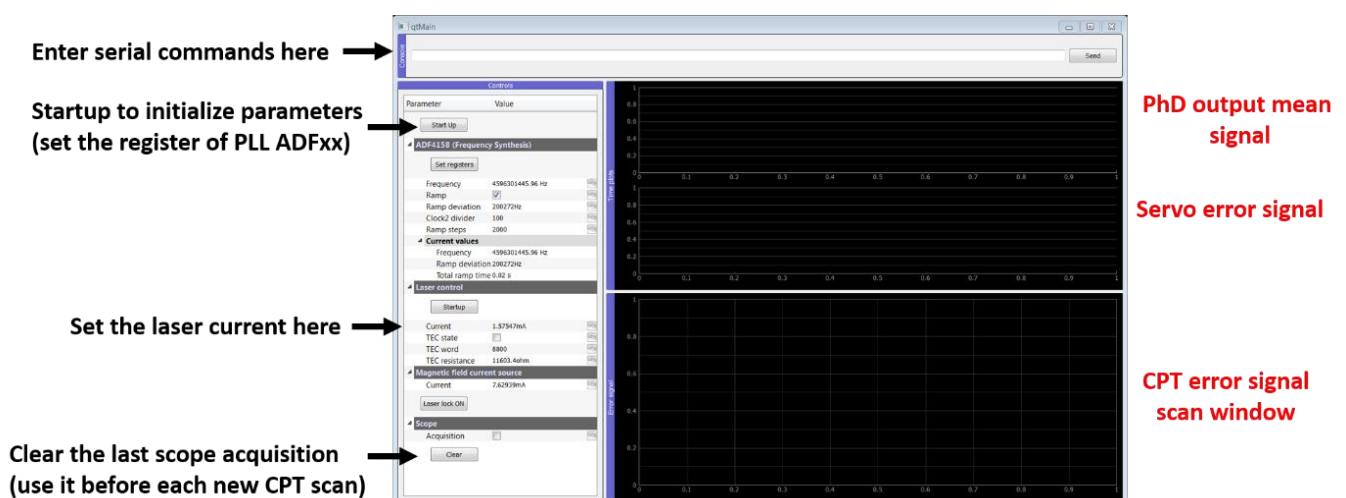


Figure 5: Program graphic interface.

The program is launched from a Jupyter Notebook which should be already running on your labwork computer.

- [1] M. Hasegawa et al., Sensors Actuators 167, 594-601 (2011).
[2] R. H. Dicke, Phys. Rev. 89, 472 (1953).

3/ Lab Works

3.1/ Open the main program interface

The graphical interface is ran from a jupyter notebook which will be already running when you start the labwork.

In case you need to restart the interface, simply chose the “Restart and Clear Output” under the “Kernel” menu, and re-run the first cell of the notebook.

With the Jupyter Notebook, you can execute code and/or plot your data in the same session.

3.2/ Initial configuration

The laser temperature setpoint has been pre-set using the Thorlabs TED200C. It is set at 22°C (11.364 kΩ) for the J clock, around 70°C (1.816 kΩ) for the TP1 clock and around 80°C (1.259 kΩ) for the TP2 clock.

For the first step, the 4.6 GHz signal power is turned off by the microwave attenuator at the output of the local oscillator card (the sliders 1 to 6 are set to “1”, see picture below).

0.1 GHz to 6.0 GHz,
0.5 dB LSB, 6-Bit,
Silicon Digital
Attenuator

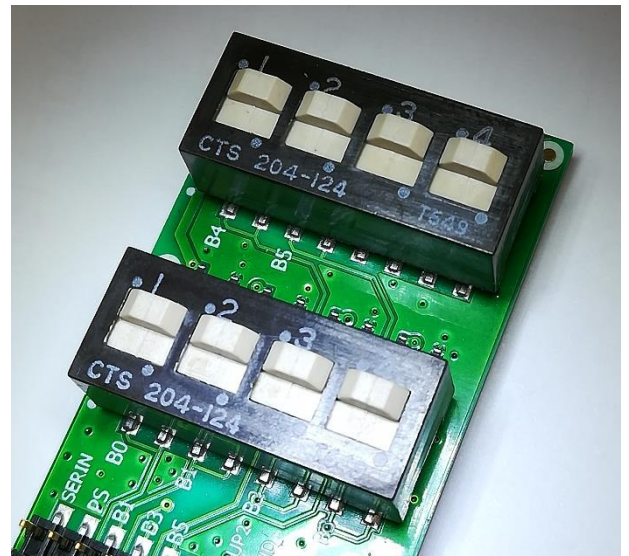
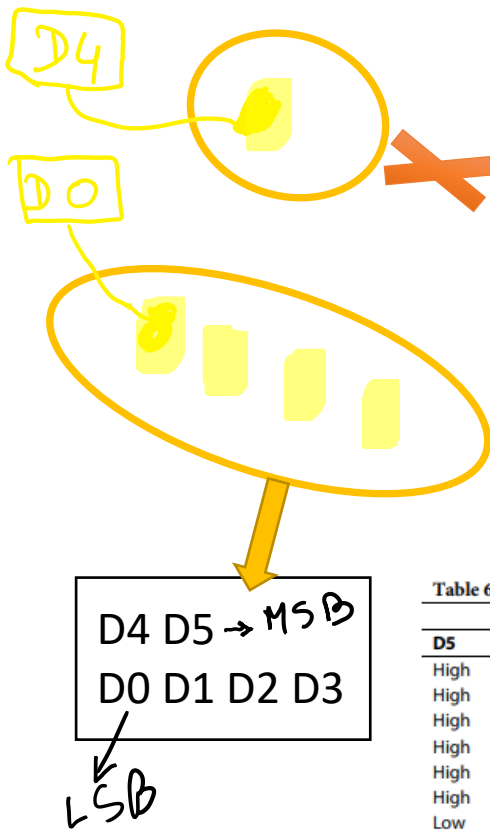


Table 6. D5 to D0 Truth Table

Digital Control Input ¹						Attenuation State (dB)
D5	D4	D3	D2	D1	D0	
High	High	High	High	High	High	0 (Reference)
High	High	High	High	High	Low	0.5
High	High	High	High	Low	High	1.0
High	High	High	Low	High	High	2.0
High	High	Low	High	High	High	4.0
High	Low	High	High	High	High	8.0
Low	High	High	High	High	High	16.0
Low	Low	Low	Low	Low	Low	31.5

¹ Any combination of the control voltage input states shown in Table 6 provides an attenuation equal to the sum of the bits selected.

3.3/ VCSEL diode laser response

Change the laser current from 0 to 1.7 mA by 0.1 mA steps and measure the photodiode output voltage with the oscilloscope. Do not surpass $I=1.8$ mA (for VCSEL protection) for the VCSEL dc current. To set the current, you can either directly enter a value in mA in the “current” box.

Store your values in your labwork dedicated .txt file, which you can open using the command window and typing:

```
G:\users\cyrus.rocjer\NextCloud\MAC control program\labwork>lvi-x.txt
```

Where x=1, 2 or J depending on your setup.

You can then use the Jupyter notebook for plotting, by restarting and clearing the kernel and then running the 2d and 3d cells of the notebook consecutively.

Identify the current value right above threshold. Set the diode current at this value and write down the digital word xxxxx sent to the Arduino in the Command Window.

3.4/ Linear spectroscopy

Tune the laser current above the lasing threshold using the laser control box interface.

The goal is now to sweep the laser frequency. For this purpose, we apply a ramp voltage onto the laser current to sweep the laser frequency. For information, the ramp is composed of 5000 pts. To do this, enter in the serial command window:

t xxxxx s

t calls the ramp function

xxxxx is the laser current (digital word) starting point, which you have measured above.

s calls a scan function

Look at the spectrum obtained on the oscilloscope. If required, tune the starting point by changing the digital word. Explain what you observe. Identify and name the different optical transitions of the Cs D₁ line. For reminder, the figure below reports the Cs D₁ line energy structure. Identify the transitions 3-3', 3-4', 4-3' and 4-4'.

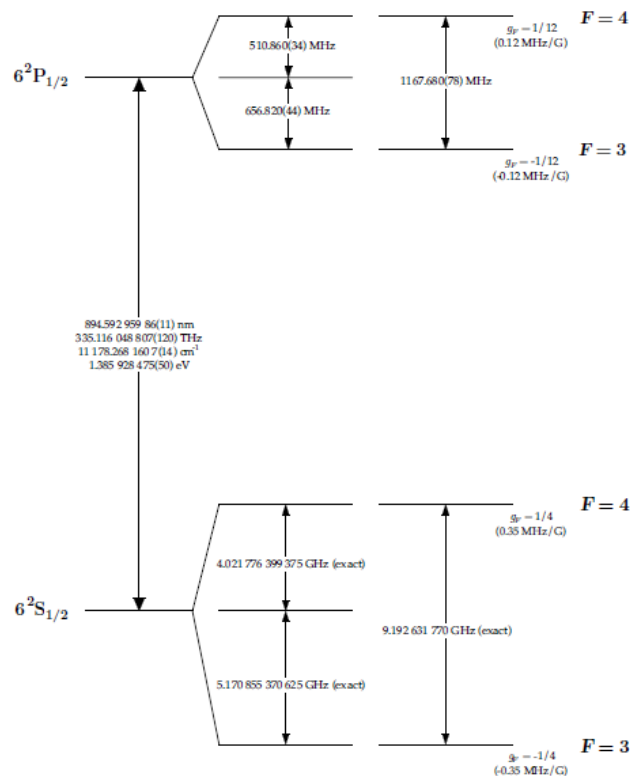


Figure 6: Cs D₁ line energy structure.Δ

Calibrate the x-axis to determine roughly the laser frequency variation for a basic digital step.

Estimate the optical absorption of the cell (the percentage of laser power absorbed by the cell). The Beer-Lambert law, assuming that we operate in an optically thin medium, could help you to estimate the actual cell temperature.

Note: one could fit this spectrum by a sum of 4 Voigt profiles to estimate the absorption lines broadening. This broadening results from the sum of the optical transition natural linewidth, the Doppler broadening and an additional broadening due to the presence of buffer gas. By using the optical density and the line broadening measurements, one can extract both the temperature and buffer gas pressure of a particular cell.

Here, you can estimate the expected Doppler broadening and see how different your measured linewidth is.

$$\Delta\nu_D = \frac{2\nu_{opt}}{c} \sqrt{(2 RT/M)\ln(2)}$$

with $\nu_{opt}=335$ THz, $R=8.31$ J/(mol.K), $M=133$ g/mol.

3.5/ Towards CPT spectroscopy

Now turn on the 4.6 GHz microwave signal and increase progressively its power using the microwave attenuator. To do this, you can set the attenuators sliders to 0, starting from the bottom-left slider. Note that you can read the actual microwave power by monitoring the spectrum analyzer. This measured power is 20 dB (20dB-coupler) lower than the one actually experienced by the VCSEL bias tee. What do you observe? Explain.

Set the microwave power (read on the spectrum analyzer) to -25 dBm.

To detect a CPT signal, we need to ensure that the laser frequency is tuned (ideally “stabilized” in a real miniature atomic clock using a lockin amplifier-based modulation-demodulation technique applied on the laser current) such that the laser is connected to a given excited state.

For this purpose, the laser frequency must be adjusted such that the photodiode output signal is tuned on the bottom of a “CPT-resonant” broadened optical line (the one that appeared between both initial doublets of the Cs D_1 line!). You first need to determine roughly the diode current value at the bottom of the central absorption line. To do so, use your knowledge of the scanning ramp.

Switch off the laser ramp (use the reset button on the clock card, shown by the red arrow in figure 4).

Apply the serial command:

9 xxxxx

9 calls a function to set the laser dc current
xxxxx is the digital word, image of the laser dc current

Check that the photodiode output voltage is well-driven to the bottom of the absorption line. If not, change the digital word by a few 10s.

Once the laser frequency is well-adjusted, you can first lock the laser using a simple linear absorption lock. To do so, type ‘3’ in the command line. Observe what happens on the photodiode signal. Right down the digital word where the laser lock has stabilized.

Once the laser frequency is well-adjusted, we can try to detect the CPT resonance by scanning the local oscillator frequency. For this purpose, Press the “Reset” button on the clock card and click the “Clear” button and enter the serial command:

b

As you can see on the spectrum analyzer, this command allows to sweep the local oscillator frequency by about 100 kHz. This value is the typical span of the “CPT error signal scan window” in the bottom of the program interface. The central frequency was set here to about 4.596340xxx GHz.

Here, you should detect the CPT signal (CPT error “demodulated” signal in fact) in the bottom CPT error signal scan window. Note that the signal to noise ratio of the CPT signal can be significantly increased by tuning finely the laser optical detuning (command 9 xxxxx where x is the laser current digital word).

Estimate the CPT signal linewidth in Hz and the CPT signal amplitude (arb. units).

Do this measurement for several values of the 4.6 GHz signal power (-29 to -24 dBm) and note for each case the CPT signal amplitude.

Note: Each time you change the microwave power, re-adjust the laser current to be on the bottom of the good optical absorption line (serial command: 9 xxxxx), click the Clear button and turn on the LO ramp (serial command b).

Plot the CPT signal amplitude (arb. units) versus the microwave power. Explain the result.

Reduce now the value of the static magnetic field current. What do you observe? Record the CPT spectrum for a few values of the static magnetic field. This measurement could help you to know the actual static magnetic field experienced by the atoms. Indeed, magnetic-sensitive Zeeman transitions are shifted by about 700 kHz/G.

From this, note that the best way to know the actual magnetic field variations experienced by the atoms is to stabilize the LO frequency onto one the magnetic-field sensitive Zeeman transition. In this case, fluctuations of the clock frequency are expected to be mainly due to this effect.

3.6/ Close the atomic clock loop

Set the microwave power at -25 dBm.

Tune the laser current to the bottom of the good absorption line (serial command: 9 xxxxx).

Enter the serial command *i xxxxx*

Enter the serial command *0*

The latter command allows to stabilize both the laser frequency and the local oscillator frequency onto the CPT resonance frequency. For both servo loops, a digital lockin amplifier technique is applied. In clock closed loop operation, the frequency synthesizer is used to scan successively on both sides of the CPT resonance. An error signal, proportional to the Raman detuning, is generated and processed in a PI controller system to correct the 10 MHz quartz oscillator pilot frequency (quartz voltage tuning). The output useful signal is the signal from the 10 MHz quartz oscillator, locked to the atoms.

Check that the servo loop is OK (stabilization of the laser current and LO frequency going to the correct frequency).

You can then measure the clock Allan deviation using the Symmetricom test setup.

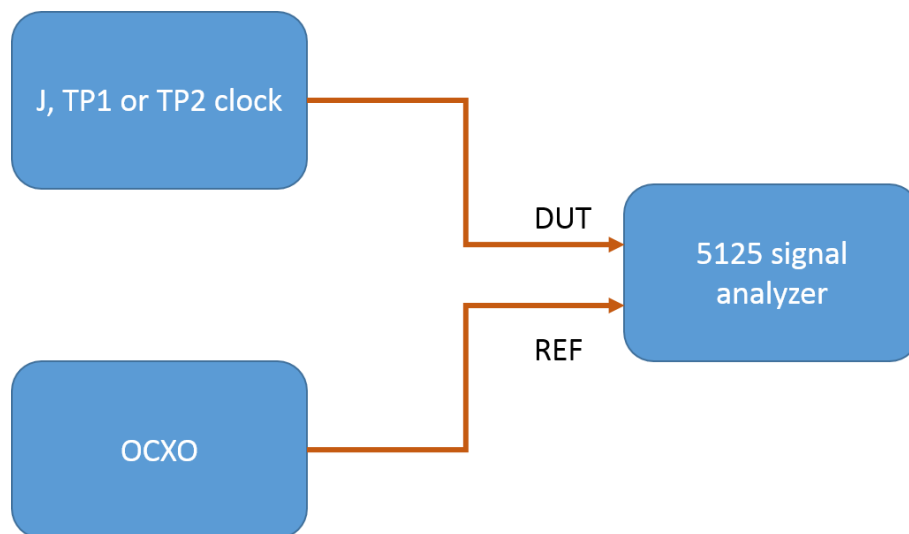


Figure 7: Clock Allan deviation measurement setup.

To do so, we will compare the labwork clocks with very stable OCXOs (oven-controlled quartz oscillators). Before measuring the clock fractional frequency instability, it is necessary to verify the OCXO performance. To do so, one can input two different OCXO signals to the 5125 signal analyzer.


You can then plug the clock LO signal at 10 MHz to the DUT port, while the OCXO signal at 5 MHz is sent to the REF port. Establish the clock short-term performance, as well as the OCXO frequency drift.

You can then compare short-term stability performances in both free-running and locked regimes.

Annex - Some corrections


3.3/ VCSEL laser response

Laser current (mA)	Photodiode output voltage (mV)
0	5.7
0.1	6.3
0.2	6.3
0.3	6.3
0.4	7.33
0.5	8.84
0.6	10.62
0.7	13.11
0.8	19.72
0.85	87.69
0.9	353
0.95	656
1	930
1.1	1480
1.2	2040
1.3	2640
1.4	3160
1.5	3600
1.6	4250
1.7	4970
1.8	5570
1.9	5730

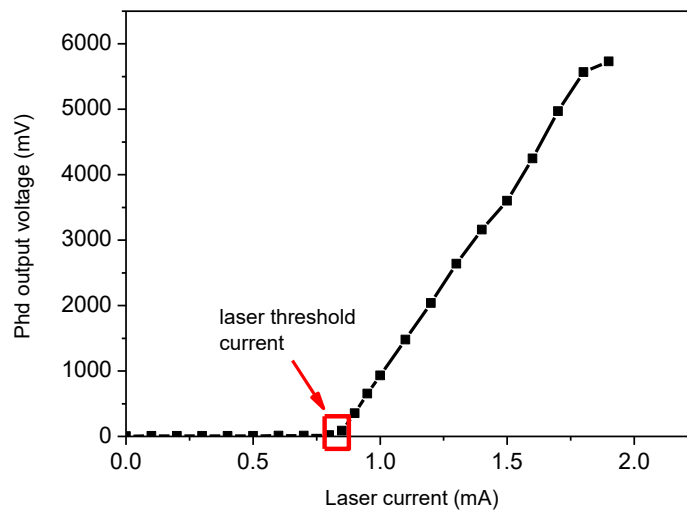

The laser threshold current is measured to be about 0.8 mA.

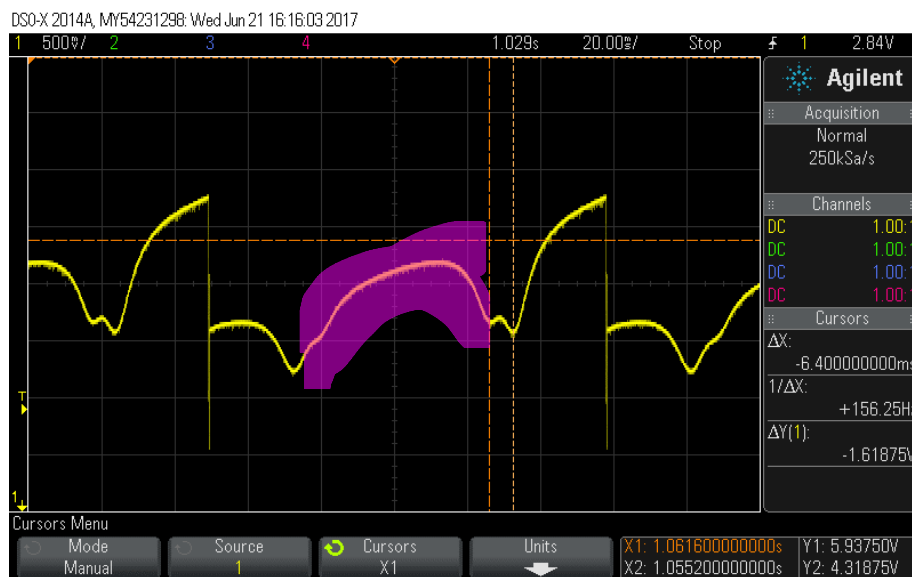3.4 / Absorption spectrum of the Cs D₁ line (without 4.6 GHz)



We find: 5000pts of the ramp = 108.8 ms.

Moreover, 1.167 GHz = 6.4 ms et 9.192631770 GHz = 54 ms.

We deduce: 5000 pts = 18.521 450 677 GHz, yielding 1 pt = 3.704 MHz of laser frequency.

3.5 / Towards CPT spectroscopy

Absorption spectrum of the Cs D₁ line (with 4.6 GHz)




with
RF

yes!

The application of the 4.6 GHz microwave signal makes appear a doublet between both initial doublets. CPT spectroscopy

Serial Command Here

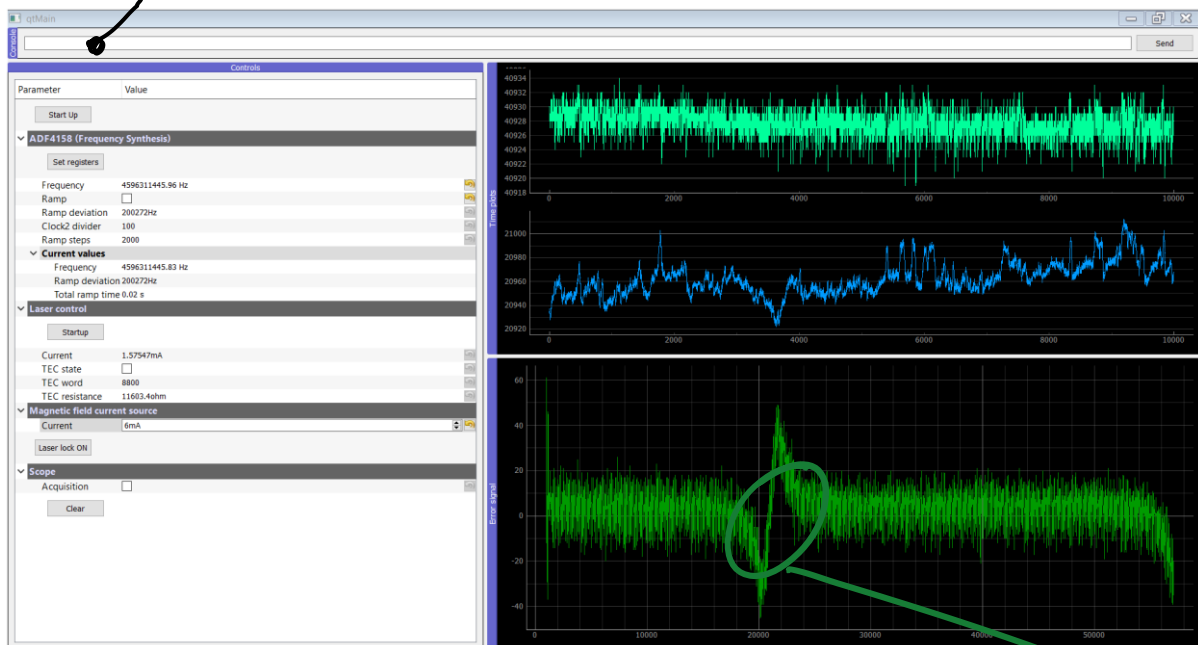


I
Q

The bottom window shows the CPT resonance on a LO frequency span of 100 kHz (@4.6 GHz).

3.6 / Close the loops.

Serial Commands reminder

Error Signal

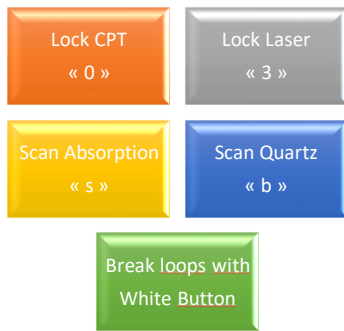

quartz
~ 20 000